
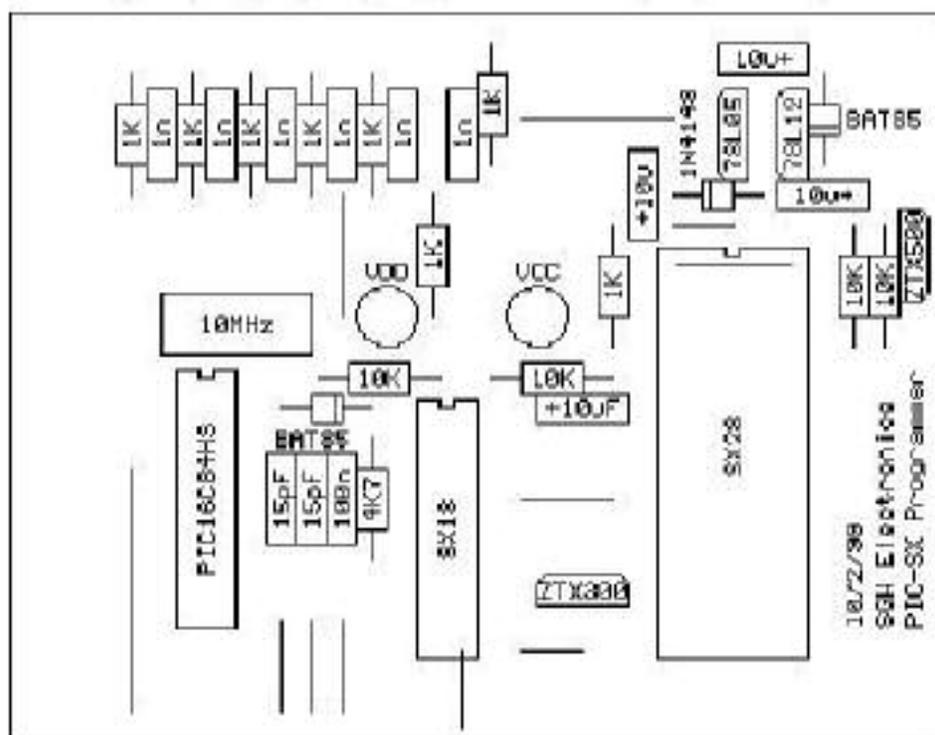


78*61mm PCB

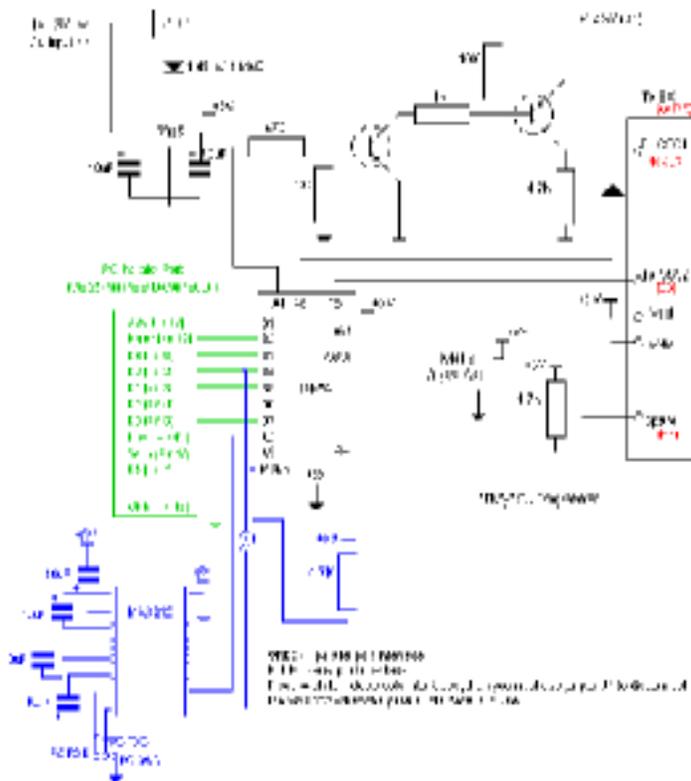- 2
- 4
- 6
- 7
- 5
- 6
- 12
- 18
- 13
- 62
- 19/29
- 80
- +15V





- 1 PIC 16F84/10
- 1 CRISTAL DE 10 MHZ
- 2 CONDENSADORES DE 15Pf
- 1 idem 100nF
- 4 idem 10uF
- 6 idem 1 nF
- 8 resistencias de 1k ohmio
- 2 bat 85
- 4 resitencia de 10 k ohmios
- 1 bc 338/25
- 1 bc 325/25
- 1 1n4148
- 1 zocalo para el 16f84
- 1 diodo led verde
- 1 diodo led rojo
- 1 conector db25 hembra
- 1 78105
- 1 78112

SOLO PROGRAMA SX
 SE NECESITARIA ADAPTA EL ZOCALO DE 28 PINES ANCHO A UNO DE 28
 PINES ESTRECHO

